

11th grade

1

01


02

03

04

01

Regulator Fundamentals

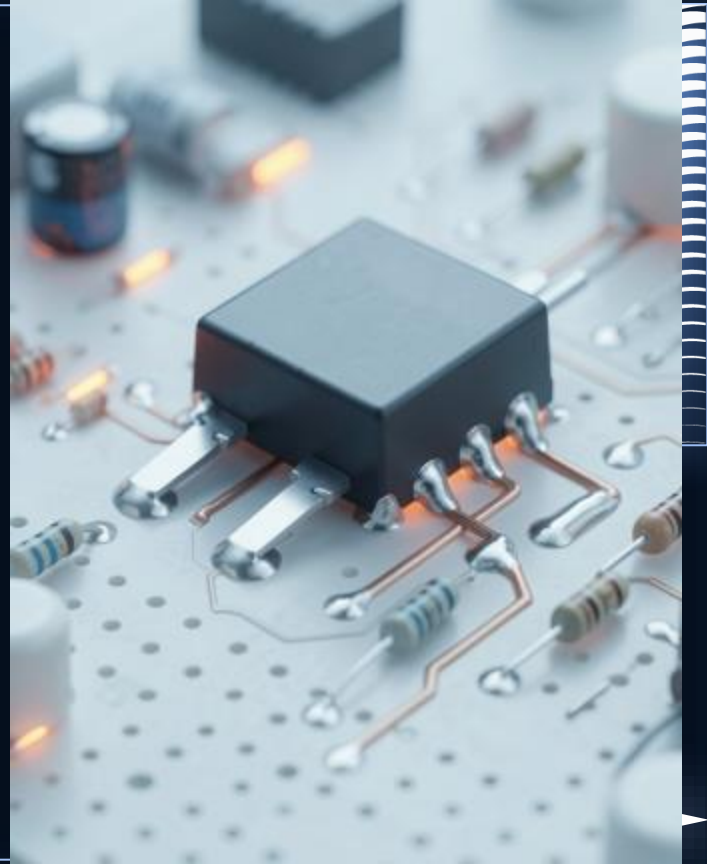


Definition & Importance

A *voltage regulator* is a device that provides a stable output voltage

Key roles: protect sensitive components, prevent malfunction from voltage swings, and enable predictable circuit behavior.

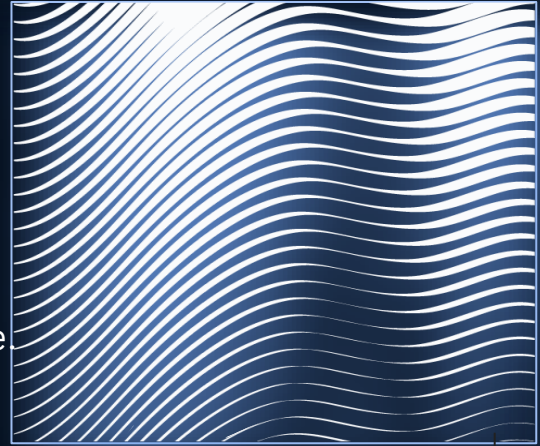Stable supply improves reliability and extends component lifespan.




Working Principles

Regulators control output via input sensing and feedback loops.

Linear types adjust pass element; switching types use energy storage and switching to achieve higher **efficiency**.

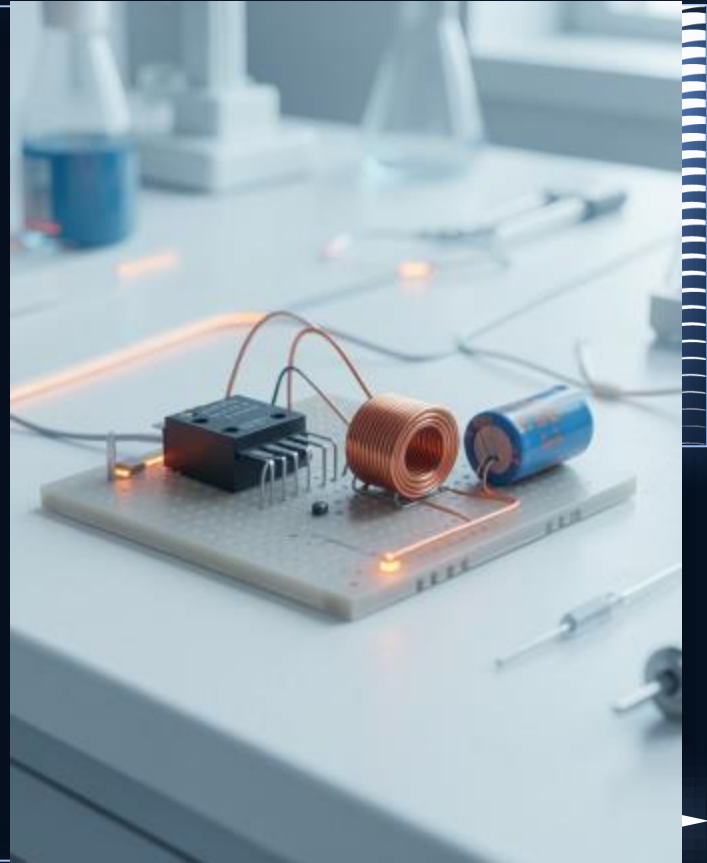Feedback monitors output and corrects deviations to maintain set voltage.





02 Applications & Design





Practical Examples


Example: 7805 linear IC powering logic from 9V with minimal components and simple filtering.

Example: Buck converter for battery-powered devices to maximize **battery life** while handling variable input.

Advantages & Tradeoffs

Linear: simple, low noise, but dissipates heat and is less efficient.

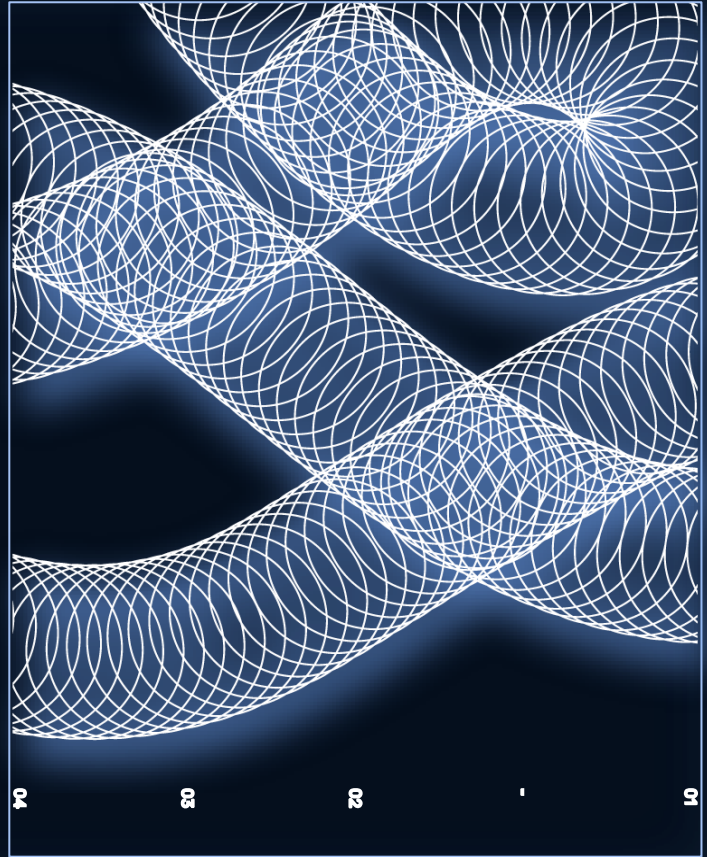
Switching: high efficiency and small thermal footprint, yet requires inductors, filtering, and EMI control.



Modern Relevance

Critical in *renewable energy* inverters, IoT nodes, and portable electronics for reliable power management.

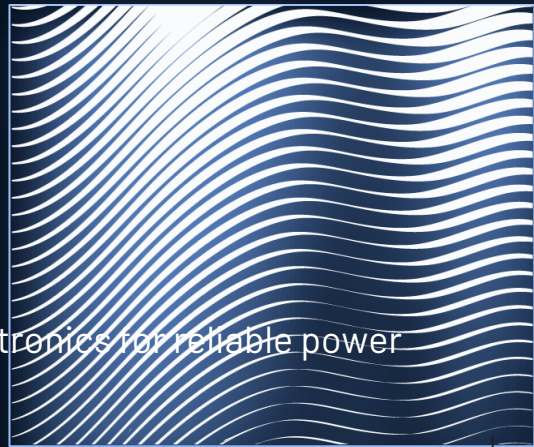
Design choices balance efficiency, size, cost, and EMI to meet contemporary device requirements.



Conclusions

Stable voltage regulation is essential for reliable electronics operation and component protection.

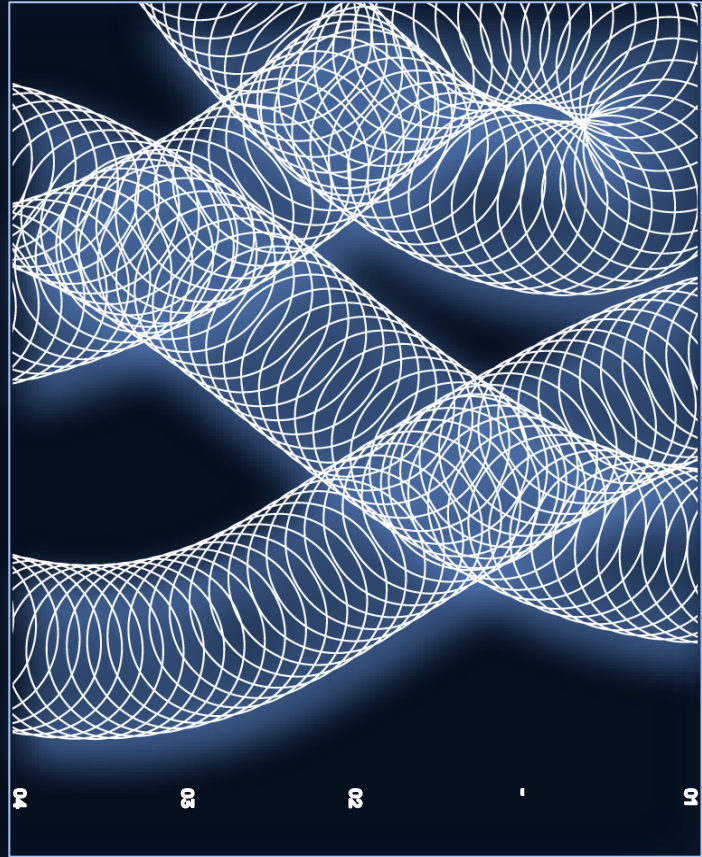Choose topology by prioritizing **efficiency**, thermal behavior, and system complexity to meet design goals.



02

Thanks!

Do you have any questions?

03

youremail@freepik.com

+91 620 421 88

yourcompany.com



04

CREDITS: This presentation template was created by
Slidesgo, including icons by Flaticon, infographics &
images by Freepik

P
r
e
s
e
n
t
a
t
i
o
n