

Electrons $\rightarrow$ negative to positive

Current $\rightarrow$ positive to negative (Ammeter) series

Electric Charge $\rightarrow$ carayan axını zamanı keçən yük -

Birlik sayı

$$Q = I \cdot t$$

$Q \rightarrow$ charge (C)

$I \rightarrow$ current (A)

$t \rightarrow$ time (s)

Potential difference $\rightarrow$ Bir yünün 1 nöqtədən başqa nöqtəyə gətirəsi zamanı yaranan enerji fərqi

P. Difference $\rightarrow$ Volts (V) $V = \frac{J}{C}$

$$V = \frac{W}{Q}$$

$W =$ work done (J) joule

$Q =$ charge (C) coulomb

$$W = N \cdot m$$

$$J = \frac{kg \cdot m^2}{s^2}$$


Electromotive force (e.m.f) $\rightarrow$ bateryanın və enerji mənbəsinin 1 güc verdiyi enerji.

$$\mathcal{E} = \frac{W}{Q} \quad (V) \quad V = \frac{J}{C}$$

$$\mathcal{E} = IR + Ir = I(R+r)$$

$$\text{Lost volts} = Ir$$

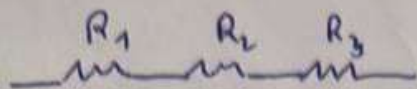Series Circuit $\rightarrow$ components connected end to end




$$I = \text{const}$$

$$R_{\text{total}} = R_1 + R_2 + R_3$$

$$V = IR$$

$$V_{\text{total}} = V_1 + V_2 + V_3$$

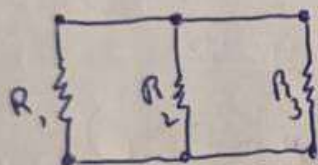Parallel Circuit $\rightarrow$ components are connected across each other's lead



$$V = \text{const}$$

$$R_{\text{total}} = \frac{R_1 \cdot R_2}{R_1 + R_2}$$

$$I_{\text{total}} = I_1 + I_2 + I_3$$

Ohm law $\rightarrow$

$$I = \frac{V}{R}$$

$$V = IR$$

$$R = 0 \Omega$$

Electricity $\rightarrow$ is movement of charge (electrons)

1) proton $\rightarrow +$ 3) neutron $- 0$ charge

2) electron $\rightarrow -$

1) Electrons move around the nucleus

2) Protons and neutrons stay in it.

$+/+$ or $-/-$ repel (Itobiyir)

$+/-$ attract (Yosunboshur)

Current $\rightarrow$ electric current is the flow of charge (elektrik)

unit $\rightarrow$ Ampere (A)

current dınasa elektronların hareketi
haraket elektron, yayılma

charges $\rightarrow \oplus \ominus$

When conductor is exposed to a potential difference,
charge carries flow

Circuit $\rightarrow$ 1) electricity flows only in a complete circuit
(closed loop)

2) electrons return to start point $(+ \rightarrow -)$

If circuit is open $\rightarrow$ no flows

Components: 1) Energy source - battery

2) Conductor - wires ~~for~~ path for current

3) Load $\rightarrow$ lamp

4) Switch $\rightarrow$ controls circuit

Shor

$$1) V = IR$$

$$V = 9V$$

$$R = 3 \text{ k}\Omega = 3000 \Omega$$

$$I = \frac{V}{R} = \frac{9}{3000} = 3 \cdot 10^{-3} = 3 \text{ mA}$$

$$2) \text{ series} \rightarrow R_{\text{total}} = 3 + 10 + 5 = 18 \cdot 10^3 \Omega$$

$$V = 9V \Rightarrow I = \frac{9}{18 \cdot 10^3} = 0.5 \cdot \text{mA}$$

$$3) U_1 = R_1 \cdot I = 3 \cdot 10^3 \cdot 500 \cdot 10^{-6} = 1.5 \text{ V}$$

$$U_2 = R_2 \cdot I = 10 \cdot 10^3 \cdot 500 \cdot 10^{-6} = 5 \text{ V}$$

$$U_3 = R_3 \cdot I = 5 \cdot 10^3 \cdot 500 \cdot 10^{-6} = 2.5 \text{ V}$$

$$1.5 + 5 + 2.5 = 9 \text{ V}$$

$$4) E = 9V$$

$$K = 1440$$

$$P = 240$$

$$t = 120 \text{ s}$$

$$E = I(R + r)$$

$$I = \frac{P}{V} = \frac{240}{120} = 2 \text{ A}$$

$$V = \frac{K}{P} = \frac{1440}{240} = 6$$

$$R = \frac{V}{I} = \frac{6}{2} = 3 \Omega$$

$$9 = 2 \cdot (3 + r)$$

$$4.5 = 3 + r$$


$$r = 1.5$$

$$5) R = \frac{V}{I} = \dots$$

$$V = \frac{K}{P} = \frac{N \cdot m}{A \cdot s} = \frac{\text{kg} \cdot \text{m}}{\text{s}^2 \cdot \text{A} \cdot \text{s}} = \frac{\text{kg} \cdot \text{m}}{\text{A} \cdot \text{s}^2}$$

$$= \frac{\text{kg} \cdot \text{m}}{\text{A} \cdot \text{s}^2}$$
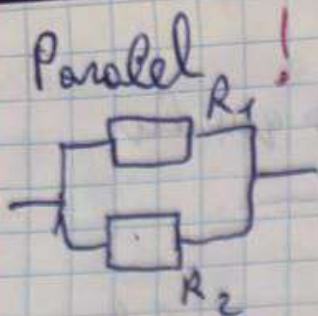
$$R = \text{kg} \cdot \text{m} \cdot \text{A}^{-2} \cdot \text{s}^{-3}$$



$$R = \frac{R_1 \cdot R_2}{R_1 + R_2}$$


$$R = \frac{R}{n}$$

$$U = \text{const}$$

$$Q = Q_1 + Q_2$$

$$A = Q = \frac{U^2}{R} \cdot t$$

$$I = \frac{U}{R}$$

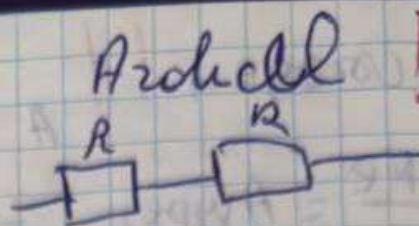

$$R = R_1 + R_2$$


$$R = n R$$

$$I = \text{const}$$

$$U = U_1 + U_2$$

$$A = Q = I^2 R t$$

$$I = \frac{U}{R}$$

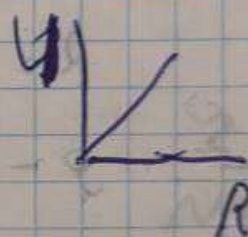

Tam dövrün üçün Q_m !!

$$\varepsilon = \frac{A_m}{Q} \approx V$$

Dövrün açılıq olanda voltmetr EMQ

qapalı olanda voltmetr gərginlik