

Physics Guide: FET-Based Amplification and Systems

Ibrahim Alakbarov

Yasin Quluzada


Tuqay Qarayev

Ramil Musazada

Verified by: Physics Teacher Azerbaijan Telman Askeraliyev (Fizika Muellimi, Azerbaijan, Baku)

FIELD EFFECT TRANSISTOR (FET): A SIMPLIFIED STUDY GUIDE

QUESTION 1: WHAT IS IT?

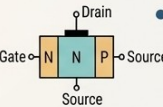

• A 'Semiconductor' device that controls current flow using an "Electric Field".


- Key terms:
 - **DRAIN** (output current leaves)
 - **SOURCE** (charge carriers enter)
 - **GATE** (controls the current)
- **Fundamental Difference:** between JFET and MOSFET and JFET controls between n-channel, and then mainly cone conduction regions.



• Text adapted from (MAGEI 0, 0). The MOSFET.


QUESTION 2: HOW DOES IT WORK?

A $V_{GS} = 0V$

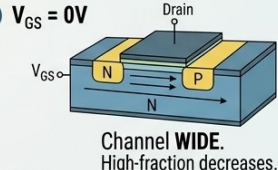


Channel **WIDE**. High-frequency decreases.

B $V_{GS} < 0V$

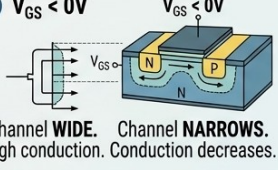

Channel **WIDE**. Channel **NARROWS**. High conduction. Conduction decreases.


C $V_{GS} = V_P$

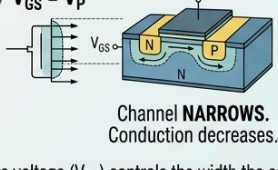


Channel **NARROWS**. Conduction decreases. **PINCHED-OFF**, stops.

Gate voltage (V_{GS}) controls the width the conducting channel.


p-channel FETs: $V_{GS} = 0V$

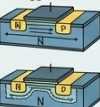

$V_{GS} < 0V$

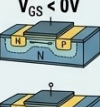


$V_{GS} = V_P$

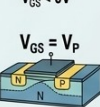


QUESTION 3: WHY IS IT USEFUL?

Ohmic (Linear) Region

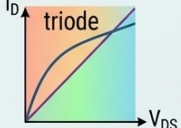


Switching Mode

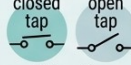

closed tap open tap

on (Saturation, on) **off** (Cut-off): man MOSFET Biasing

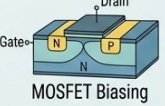The Ohmic Region. It works like a variable resistor.



Amplification



Amplification JFET characteristics and parameters.

Key Parameters (Formula Ref) Drain Definition I_{DSS} = Influential as between definition

$g_m = \frac{\Delta I_D}{\Delta V_{GS}}$ (at constant V_{DS}) Drain-to-Source saturation current (max current)

g_m = Transconductance

I_{DSS} = Zero-Gate-Voltage Drain (current current) Zero-Gate-Voltage Drain Current

Comprehensive Study on Field Effect Transistors (FET)

1. Introduction to Field Effect Transistors

A Field Effect Transistor (FET) is a three-terminal semiconductor device that uses an electric field to control the flow of current. Unlike Bipolar Junction Transistors (BJTs), which are current-controlled, FETs are voltage-controlled devices. This fundamental characteristic results in a very high input impedance, making them ideal for modern electronic applications, ranging from signal amplification to high-speed switching in integrated circuits.

Key Terminology

- **Source (S):** The terminal through which majority charge carriers enter the conducting channel.
- **Drain (D):** The terminal through which charge carriers leave the channel. The current flowing from drain to source is denoted as I_D .
- **Gate (G):** The control terminal. By applying a voltage to the gate, the width of the conducting channel is modulated, thus controlling the current.

2. Operational Principles and Channel Modulation

The core operation of a FET revolves around the modulation of the conducting channel between the source and the drain.

$V_{GS} = 0V$: Maximum Conduction

When the Gate-to-Source voltage (V_{GS}) is zero, the channel is at its maximum width. In an n-channel JFET, this allows a maximum flow of electrons, resulting in the maximum drain current, known as I_{DSS} (Drain-to-Source Saturation Current).

$V_{GS} < 0V$: Channel Narrowing

As a negative voltage is applied to the gate ($V_{GS} < 0V$), the depletion regions around the PN-junction expand. This physical expansion reduces the effective width of the n-type channel, increasing resistance and decreasing the drain current flow.

$V_{GS} = V_P$: Pinch-Off Point

When the gate voltage reaches a specific negative value known as the Pinch-off Voltage (V_P), the depletion regions meet. At this stage, the channel is completely obstructed, and the drain current effectively drops to zero. This is referred to as the "cut-off" state.

3. Operating Regions and Applications

FETs operate in different regions depending on the applied voltages, each suitable for specific functions:

- **Ohmic (Linear) Region:** In this region, the transistor acts as a voltage-controlled variable resistor. It is primarily used in signal processing where precise resistance control is required.
- **Saturation Region:** Here, the drain current remains relatively constant despite changes in V_{DS} . This is the primary region for amplification, where small changes in gate voltage lead to significant changes in output.
- **Cut-off Region:** The device acts as an open switch, allowing no current to pass.

Practical Use Cases

1. **Switching:** Due to their fast response times, MOSFETs are the backbone of digital logic gates and power electronics.
2. **Amplification:** FETs provide high gain and low noise, making them excellent for radio frequency (RF) and audio pre-amplifiers.
3. **Impedance Matching:** Their high input impedance allows them to interface between high-impedance sensors and low-impedance loads without signal loss.

4. Key Parameters for Analysis

To evaluate the performance of a FET, two primary parameters are analyzed:

- **Transconductance (g_m):** Defined as the ratio of the change in drain current to the change in gate voltage ($\Delta I_D / \Delta V_{GS}$). it represents the gain of the device.
- **I_{DSS} :** The maximum current the device can handle when the gate is shorted to the source.

5. Comparative Analysis: JFET vs. MOSFET

While all FETs operate on the principle of an electric field, the physical construction leads to different performance characteristics.

Junction Field Effect Transistor (JFET)

A JFET consists of a channel of semiconductor material with a PN-junction on the side.

- **Input Impedance:** High, but lower than a MOSFET because the gate is a reverse-biased diode.
- **Operating Mode:** Only works in Depletion Mode (it is "normally on" and you must apply voltage to turn it off).
- **Robustness:** Generally more resistant to static electricity (ESD) than MOSFETs.

Metal-Oxide-Semiconductor FET (MOSFET)

MOSFETs use an ultra-thin layer of silicon dioxide (SiO_2) as an insulator between the gate and the channel.

- **Input Impedance:** Extremely high (essentially infinite at DC) due to the insulating layer.
 - **Operating Modes:** Available in Depletion (normally on) and Enhancement (normally off). Most modern digital circuits use Enhancement-mode MOSFETs.
 - **Scalability:** They can be made incredibly small, which is why billions of them are packed into a single CPU or smartphone chip.
-

6. Detailed Real-World Examples and Applications

A. The Common-Source Amplifier

In audio equipment, FETs are used in a "Common-Source" configuration. Because of their high input impedance, they do not "load" the previous stage of the circuit. This results in a very clean, low-noise amplification of weak signals from microphones or musical instrument pickups (like electric guitar pre-amps).

B. CMOS Technology in Computing

Modern computers use CMOS (Complementary Metal-Oxide-Semiconductor) technology. This involves using pairs of p-type and n-type MOSFETs together.

- **Example:** In a processor, when a logic gate is not switching, one of the transistors is always "off," meaning almost zero power is consumed. This is why laptops and phones can have long battery lives despite having billions of transistors.

C. Power Electronics (Electric Vehicles and Solar)

Power MOSFETs are designed to handle high voltages and currents.

- **Example:** In an Electric Vehicle (EV) inverter, MOSFETs act as high-speed switches to convert DC battery power into AC power for the motor. Their ability to switch thousands of times per second with minimal heat loss makes them more efficient than older bipolar technologies.
-

7. Performance Limitations (The "Real World" Constraints)

No electronic component is perfect. When writing your document, consider these trade-offs:

- **Temperature Sensitivity:** As the temperature increases, the mobility of the charge carriers in a FET decreases, which can reduce the drain current.
- **Capacitance:** The insulating layer in a MOSFET acts like a small capacitor. At very high frequencies, this capacitance can slow down the switching speed.
- **Static Sensitivity:** Because the SiO_2 layer in a MOSFET is so thin, a small spark of static electricity can puncture the insulation and permanently destroy the device.